

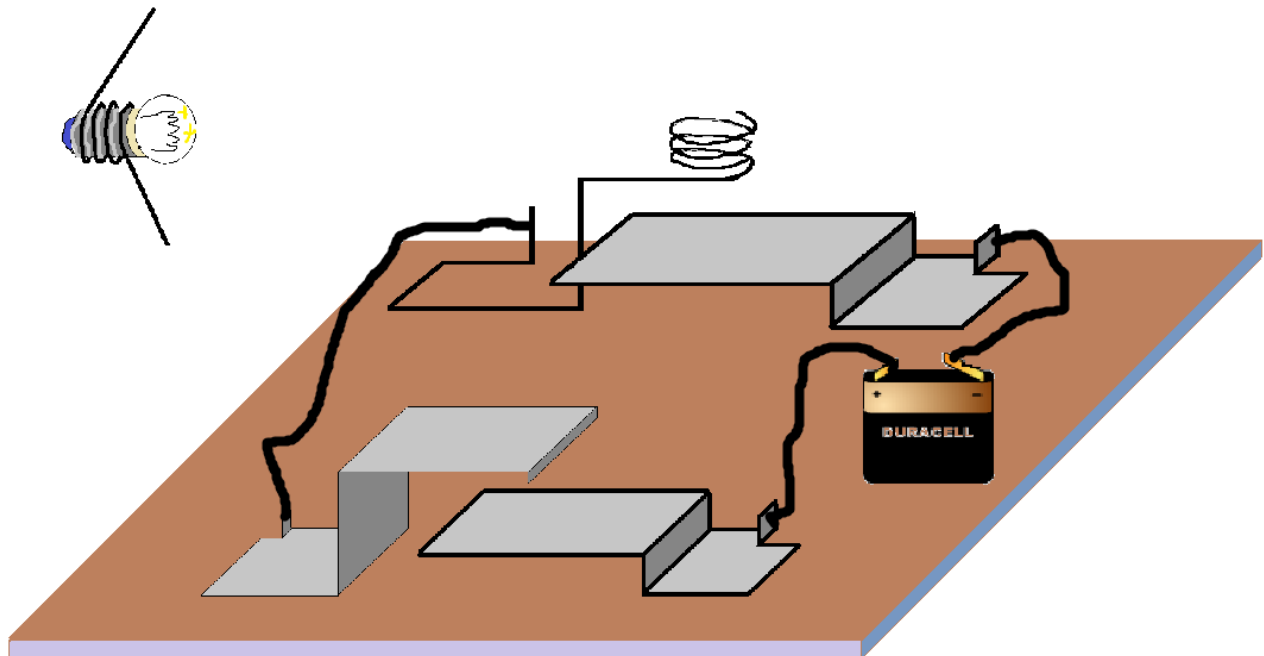
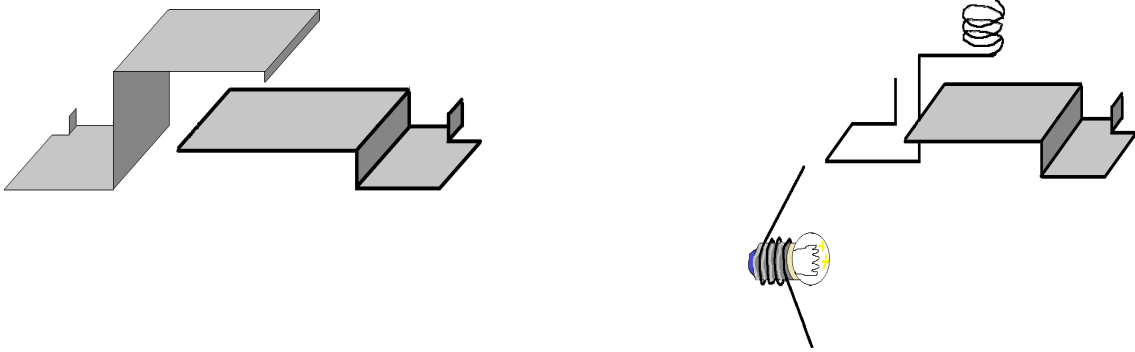


# ELECTRICITY CIRCUITS IN THE WORKSHOP

## 1.- Push-button and lamp holder

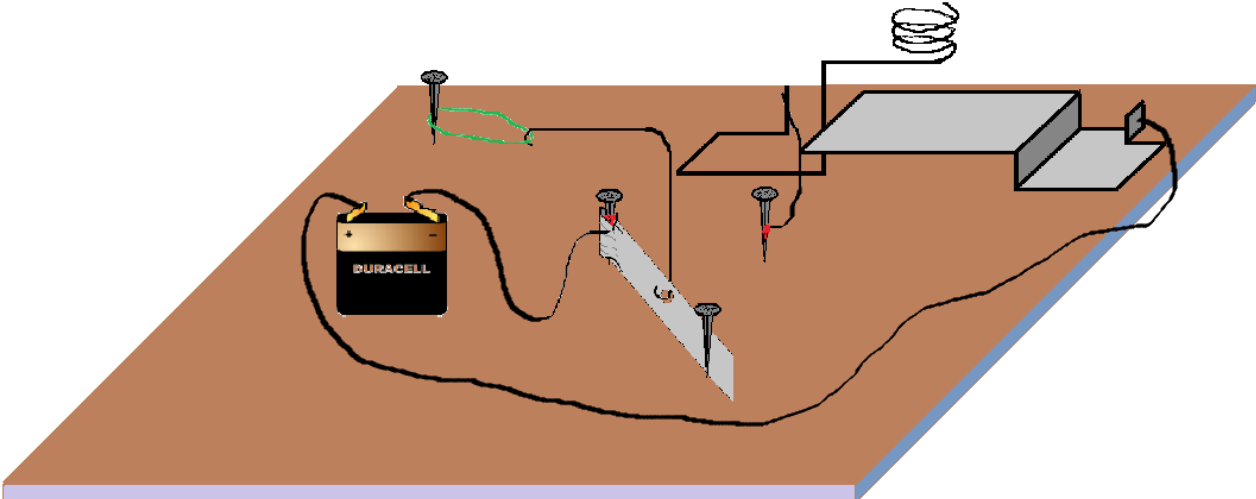

2.- Clis-clas switch

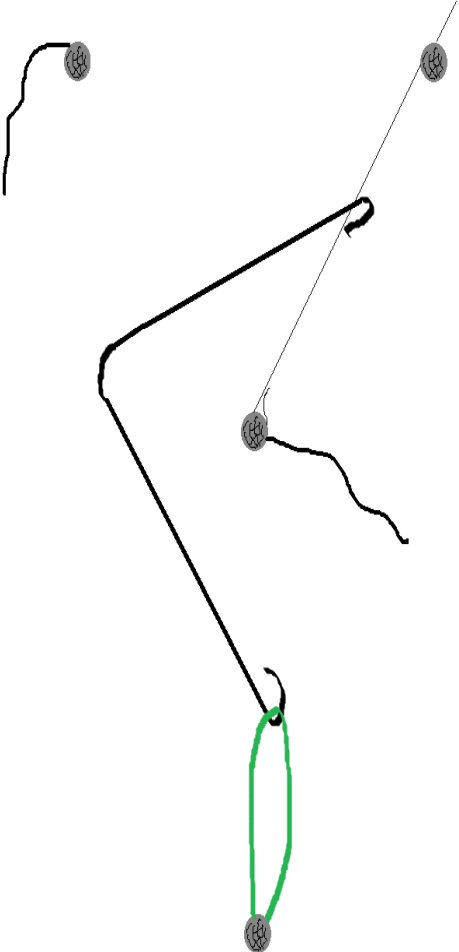

3.- Inverting direction of rotation in a motor

